



R-ser:

12 Ohm:	300 mA @ 1W	LED=8.40V	
10 Ohm:	355 mA @ 1.3W	LED=8.45V	
9 Ohm:	391 mA @ 1.4W	LED=8.48V	-> 3.3W = is as used
6 Ohm:	570 mA @ 1.95W	LED=8.58V	

AQUARIUM LED FRAME #2
Øyvind Teig (Trondheim)
10.2019